 


TUTORIAL

MY FIRST FPGA DESIGN

Tristan Gingold - tgingold@free.fr - FOSDEM'18


IT'S A TALK ABOUT HARDWARE!



Things like
that...

There are many talks
at FOSDEM about software.
Try a different room


IT'S A TALK ABOUT CHIP DESIGN

 

This


This is a PCB
(Printed Circuit Board)
KiCad is a tool to design
boards, you also need
electronic knowledge

MORE SPECIFICALLY, DIGITAL CHIPS

 

See the difference ?

DESIGNING AN IC IS COMPLEX...

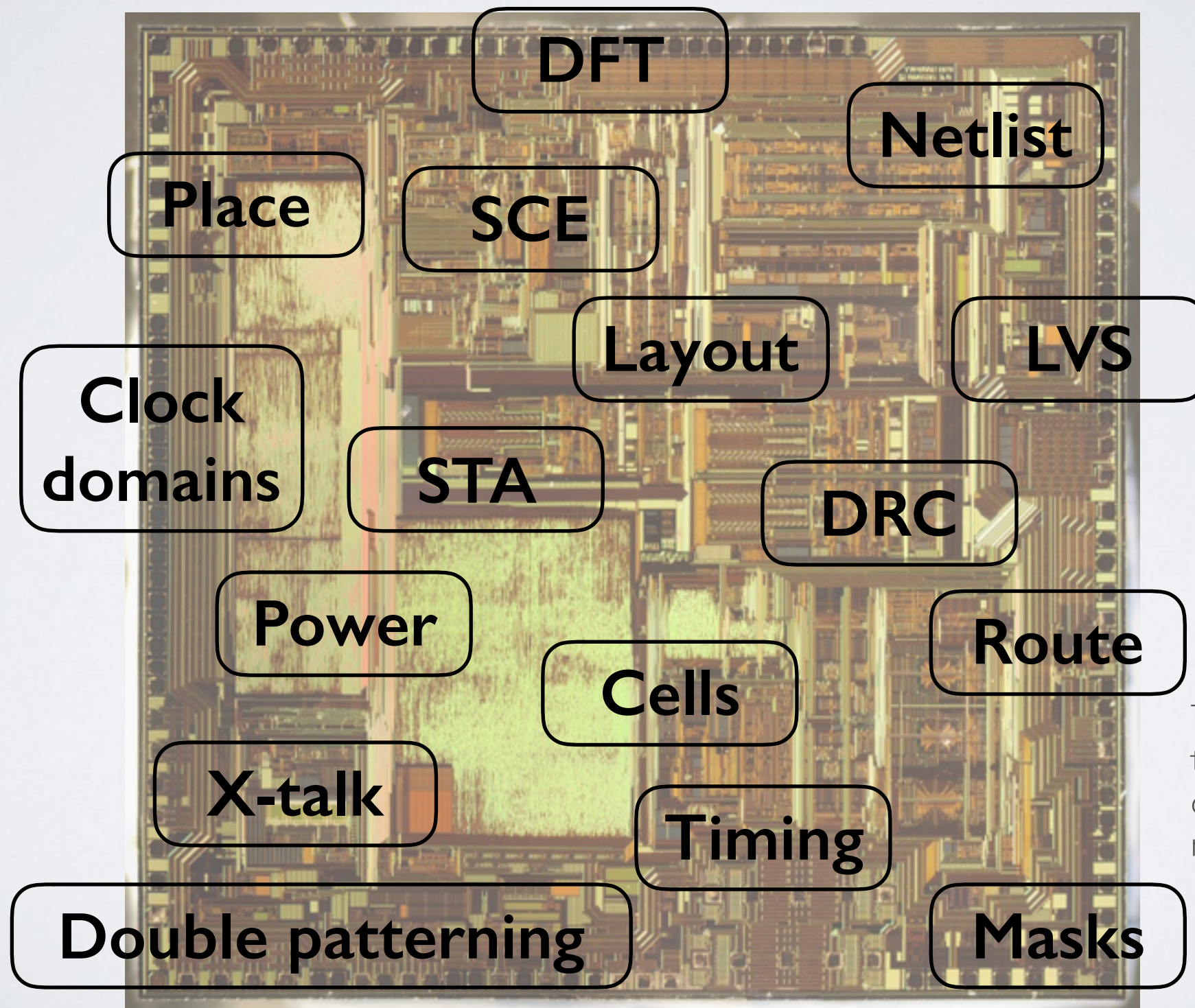


There aren't many OSS
tools for ASICs.
qflow
magic VLSI

... AND VERY EXPENSIVE




ASML lithography machine
Expect \$\$\$ for the first chip...

BUT SOME ARE PROGRAMMABLE!

 


Normal chip

 

FPGA

There are other kinds of
programmable circuits:
Gate array
CPLD
...

FPGA ARCHITECTURE

 


That's a very simple view...

Most FPGAs also have PLL, memories, multipliers, or even SERDES/PCI-e blocks.

See FPGA databooks

DIGITAL IS ABOUT 0 AND 1

 

That's simple !
Assuming you
know about
binary
computation

For analog design,
see gnuicap, qucs, spice...

(There are always
analog parts in a
circuit)

DIGITAL IS ABOUT LOGIC


BASIC OPERATIONS

NOT gate
 $D = \sim A$

OR gate
 $Z = D \mid E$

Inputs


Output

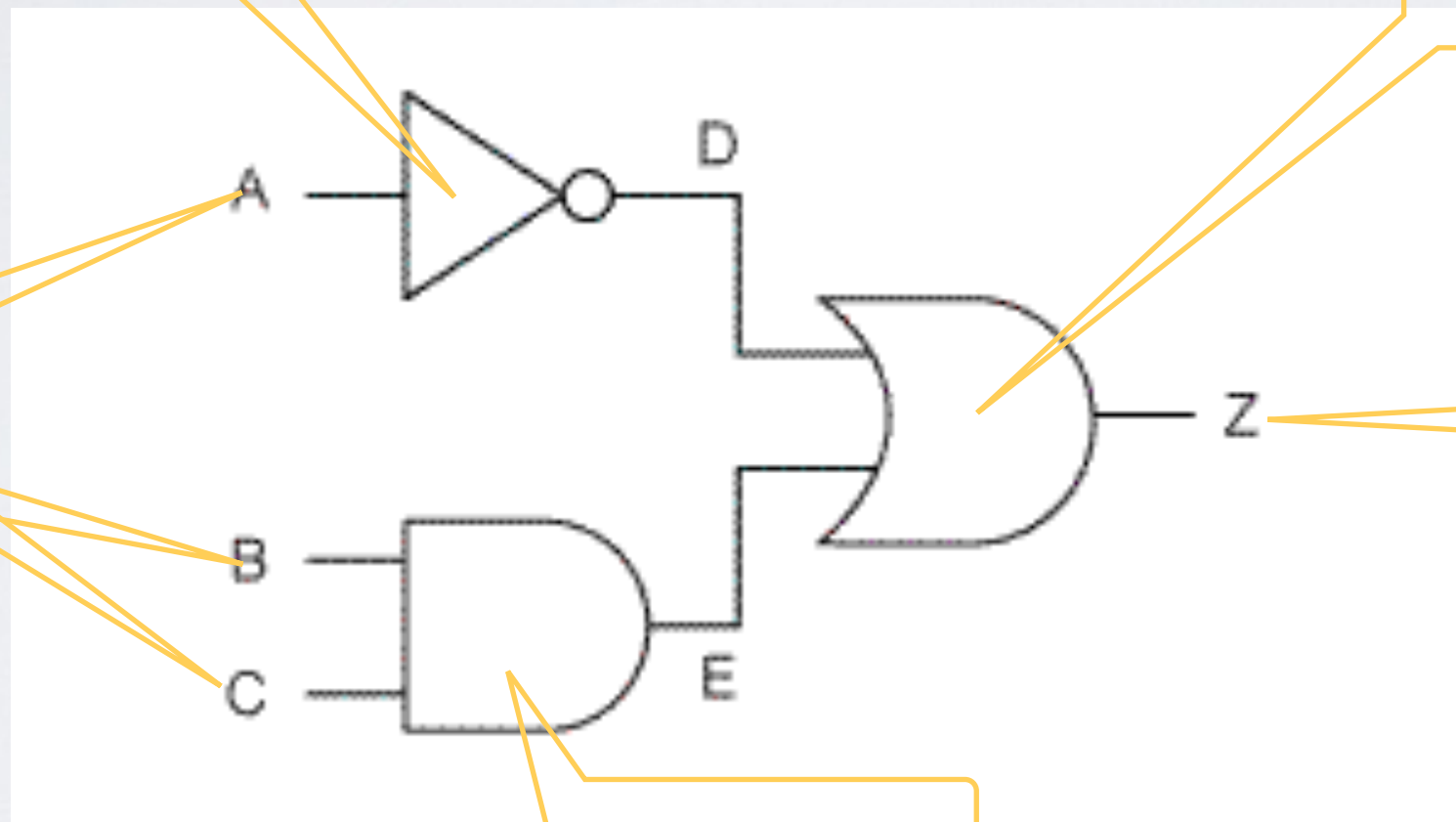

bbc.co.uk

AND gate
 $D = B \& C$

COMBINE THEM!

 


[wikipedia.org](https://en.wikipedia.org/wiki/XOR_gate)

$$Q = A \wedge B$$



Symbol for XOR gate

OR DO MATH (ONE BIT)

 


[wikipedia.org](https://en.wikipedia.org/wiki/Exclusive_OR)

$$\begin{aligned} Q &= A \wedge B \\ &= A + B \\ &= A \sim B \end{aligned}$$


A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

THE ADDER

 


S : SUM
C : CARRY


wikipedia.org

 

Full Adder

 

MULTIPLE BIT ADDER

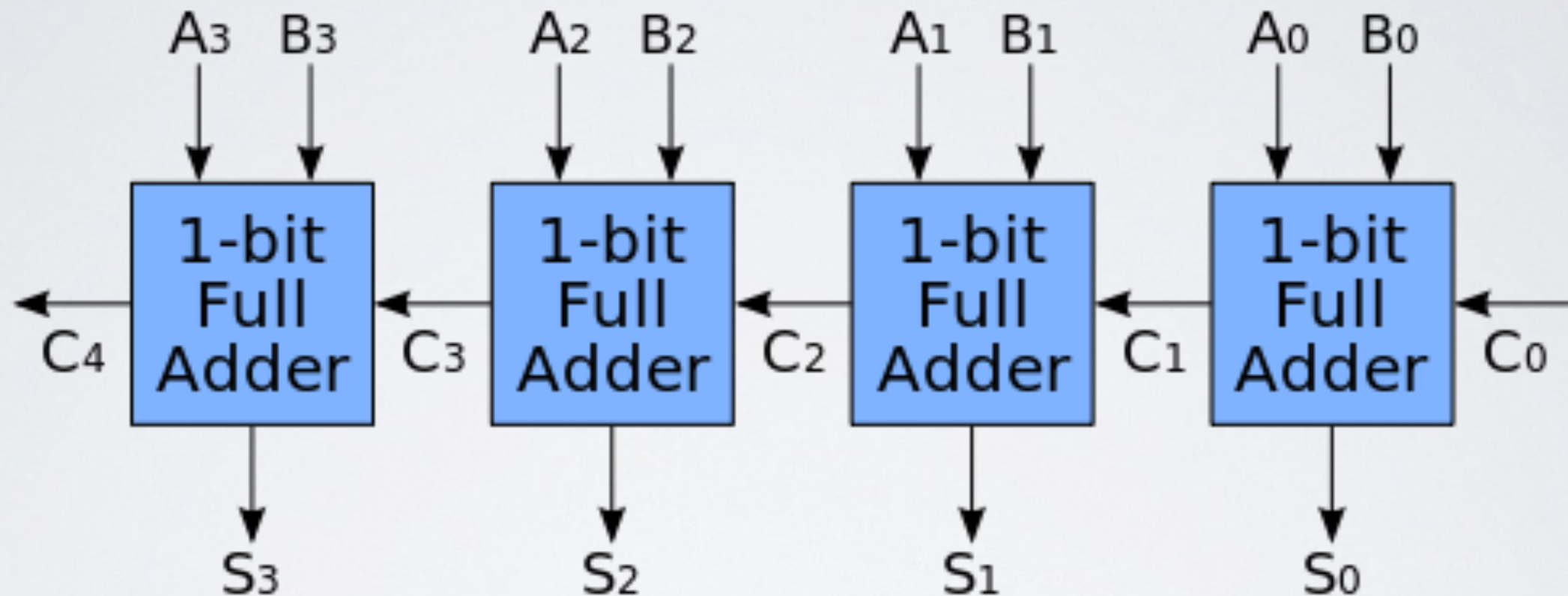


$$S = A + B$$

There are more efficient way to design large adders
Search for Digital Logic Architecture


IF YOU CAN ADD, YOU CAN MULTIPLY!

$$P = A * B$$

 

There are more efficient way
to design multipliers

 
YOU CAN DESIGN ANY LOGICAL/ARITH FUNCTION



Well, many functions...

But this is not very efficient (can take a lot of gates)

MORE POWERFUL: RECURSION!

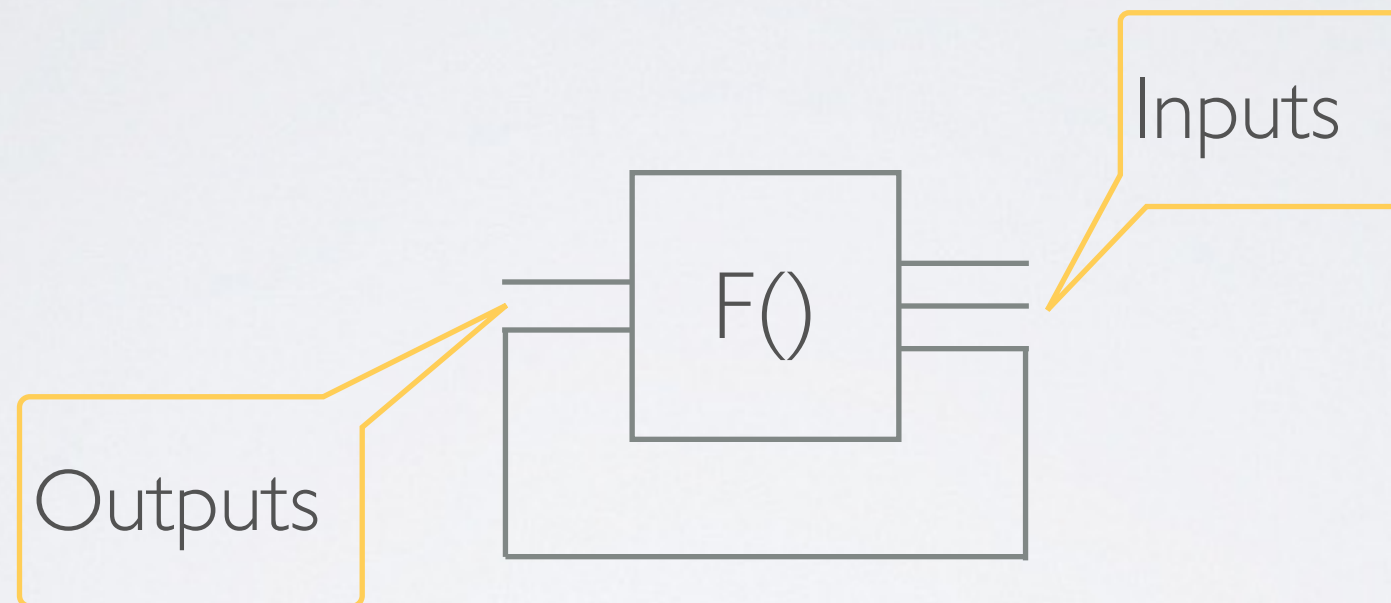


In math,
recursion is very powerful.

In digital design,
it doesn't work directly!

TIMING SYNCHRONISATION

Do you remember the full adder ?

 


wikipedia.org

It takes time for a signal to propagate through gates.
(due to capacities).



So the arrival times at S and C_{out} differ.

TIMING DIAGRAM

 

What you expect:

What you get:

  

Thanks to <http://wavedrom.com/editor.html>

Outputs are not available at the same time.

SYNCHRONOUS DESIGN

You can try to balance paths, but:

- It's very hard
- propagation time depends on too many factors

You can use a logic that is not affected by delay variation (like gray code), but:


- works only in some cases.

Rule #1:

no direct loop/feedback

So how to do ?

SYNCHRONOUS DESIGN

 

DIGITAL DESIGN

It's a mix of:

- logic gates
- flip flops

There are other way to synchronise
(latch, falling edge, double edge...)

It is possible to use schematic editors, but

- tedious
- doesn't scale well

Use an HDL

Hardware Description Language

I will use VHDL

MY FIRST DESIGN BLINKING LEDS



Using OSS tools:

- ghdl
- yosys
- arachne-pnr
- iceStorm

Target: Lattice iCEstick

~ 22 euros

Supported by OSS tools

VHDL: EXTERNAL INTERFACE

boilerplate

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
-- Led positions
```

```
-- I      D3  
-- r  
-- D      D2  D5  D4  
-- A  
--  
--      D1  
--
```

Comment
(to not forget
leds position)

interface

```
entity leds is  
  port (clk : in std_logic;  
        led1, led2, led3, led4, led5 : out std_logic);  
end leds;
```

Input: clock
(externally generated 3Mhz)

outputs: leds

INTERNALS

Internals

Internal
wire

```
architecture blink of leds is
    signal clk_4hz: std_logic;
begin
    process (clk)
        variable counter : unsigned (23 downto 0);
    begin
        if rising_edge(clk) then
            if counter = 2_999_999 then
                counter := x"000000";
                clk_4hz <= not clk_4hz;
            else
                counter := counter + 1;
            end if;
        end if;
    end process;

    led1 <= clk_4hz;
    led2 <= clk_4hz;
    led3 <= clk_4hz;
    led4 <= clk_4hz;
    led5 <= clk_4hz;
end blink;
```

Process:
concurrent
execution,
triggered on
clk

concurrent
assignments

SYNTHESIS

Translating (or compiling) sources to gates (netlist)

First, analysing sources:

```
ghdl -a leds.vhdl  
ghdl -a blink.vhdl
```

Synthesis:

```
yosys -p 'ghdl leds; synth_ice40 -blif leds.blif'
```

unit name


output file

synthesis script

frontend command

PLACE & ROUTE

Allocate resources on the FPGA

 

device

input

```
arachne-pnr -d 1k -o leds.asc -p leds.pcf leds.blif
```

output

place file

```
set_io led1 99
set_io led2 98
set_io led3 97
set_io led4 96
set_io led5 95
set_io clk 21
```

IC pin #

PROGRAM

Write into the FPGA



USB interface

flash

Create the binary file:

```
icepack leds.asc leds.bin
```

Write to flash:

```
iceprog leds.bin
```

The FPGA is automatically reset and then load the new config

TOOLS USED

Synthesis:

<http://www.clifford.at/yosys/>

VHDL front-end:

<https://github.com/tgingold/ghdlsynth-beta>

<https://github.com/tgingold/ghdl>

Place and route:

<https://github.com/cseed/arachne-pnr>

iCE40 tools:

<http://www.clifford.at/icestorm/>

QUESTIONS ?