

# Introduction to Formal Verification of Digital Circuits

Cesar Strauss

FOSDEM 2024

# Why Formal Verification?

- A tool for finding bugs
- Complementary to simulation
- Helps finding corner cases
- ... triggered by specific sequences of events

# Comparison with traditional debugging concepts

formal	traditional
Cover	Simulation
Bounded Model Check	Unit test
k-Induction	Test fixture?
Exhaustive search	random test cases
synthesizable test-bench	can be procedural
“assume” inputs	test vectors
“assert” outputs	“assert” outputs

- HDL: includes assertions
- SBY: work plan, drives the process
- Yosys: synthesizes to logic functions:
  - state  $s$ : contents of all registers and inputs
  - initial predicate:  $I(s)$
  - transition relation  $T(s_1, s_2)$
  - assertions:  $P(s)$
- yosys-smtbmc: proves correctness or outputs a trace
  - exhaustive search for a path from the initial state to a bad state
  - if not found, the design is correct
  - if found, output an error trace



# Unbounded inductive proof

- bad trace:




$$I(s_0)P(s_0) \wedge T(s_0, s_1)P(s_1) \wedge \cdots \wedge T(s_{k-1}, s_k)\overline{P(s_k)}$$

- $k \leftarrow 0$
- base case: no path from initial state leads to a bad state in  $k$  steps
- if base case fails, report the bad trace
- inductive case: no path ending in a bad state can be reached in  $k+1$  steps
- if inductive case fails,  $k \leftarrow k + 1$  and repeat
- otherwise, proof is complete, circuit is safe.


# Single register with feedback

  

# Registered output with internal state

   


# Registered output with enable

 





# Flip-flop with input

 

# Verifying a flip-flop

 
 
# Complete flip-flop with input and enable



## Code for simple register with feedback

```
module simple(input clk);  
  
reg r = 0;  
  
always @(posedge clk)  
    r <= r;  
  
`ifdef FORMAL  
always @*  
    assert(!r);  
`endif
```

```
[options]
```

```
mode prove
```

```
depth 1
```

```
[engines]
```

```
smtbmc yices
```

```
[script]
```

```
read_verilog -formal simple.v
```

```
prep -top simple
```

```
[files]
```

```
simple.v
```

## Output (simplified)

```
$ sby simple.sby
```

```
induction: Trying induction in step 1..
```

```
induction: Trying induction in step 0..
```

```
induction: Temporal induction successful.
```

```
basecase: Checking assumptions in step 0..
```

```
basecase: Checking assertions in step 0..
```

```
basecase: Status: passed
```

```
summary: engine_0 (smtbmc yices) returned pass  
for induction
```

```
summary: engine_0 (smtbmc yices) returned pass  
for basecase
```

```
summary: successful proof by k-induction.
```

```
DONE (PASS, rc=0)
```

## Flip flop with enable (1/2)

```
from nmigen.asserts import Assert, Assume, Past
from nmutil.formaltest import FHDLTTestCase
from nmigen import Signal, Module
import unittest

class Formal(FHDLTTestCase):
    def test_enable(self):
        m = Module()
        r1 = Signal()
        r2 = Signal()
        s = Signal()
        en = Signal()
        m.d.sync += [r2.eq(r1), r1.eq(r2)]
        with m.If(en):
            m.d.sync += s.eq(r1 & r2)
```

## Flip flop with enable (2/2)


```
m.d.comb += Assert(~s)
m.d.sync += Assume(Past(en) | en)
m.d.comb += Assert(~r1 & ~r2)
self.assertFormal(m, mode="prove", depth=5)
```

```
if __name__ == '__main__':
    unittest.main()
```



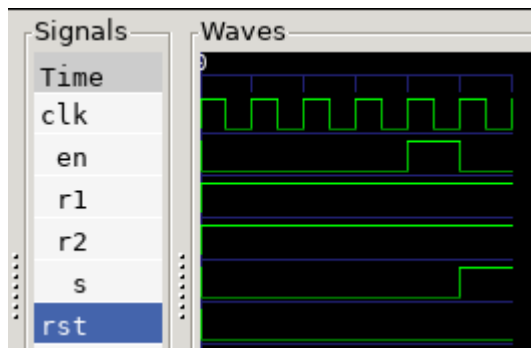
# Induction failure example


```
summary: engine_0 returned pass for basecase  
summary: engine_0 returned FAIL for induction  
DONE (UNKNOWN, rc=4)
```


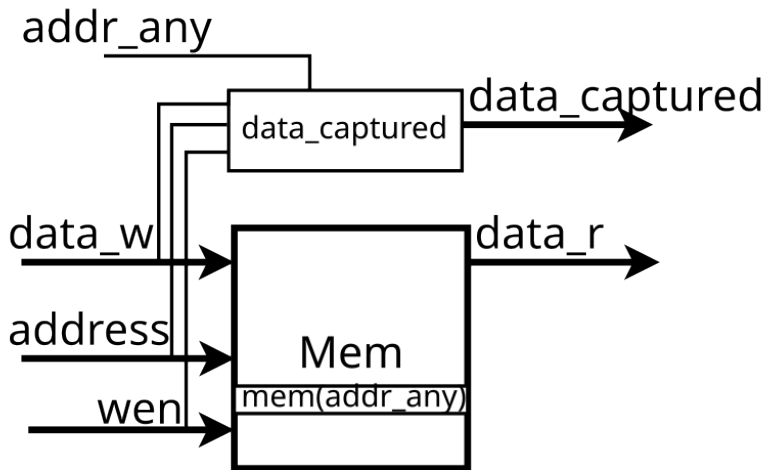
# Verifying memories with a “victim address”



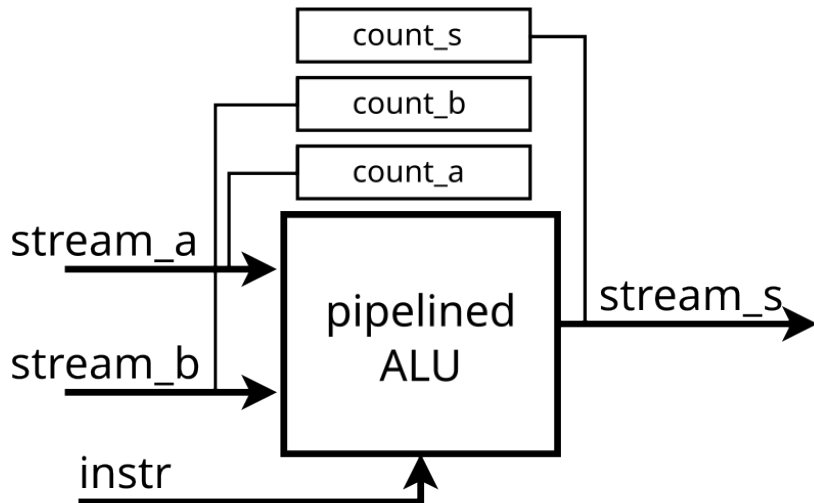
# Verifying streams with transaction counters


 
# Dynamic SIMD

exp-a : ....0....0....0.... 1x 32-bit  
exp-a : ....0....0....1.... 1x 24-bit plus 1x 8-bit  
exp-a : ....0....1....0.... 2x 16-bit  
...  
...  
exp-a : ....1....1....0.... 2x 8-bit, 1x 16-bit  
exp-a : ....1....1....1.... 4x 8-bit



# The End

## Thank you

## Questions?

- Discussion: <http://lists.libre-soc.org>
- Libera IRC [#libre-soc](#)
- <http://libre-soc.org/>
- <https://libre-soc.org/resources/>
- <http://nlnet.nl/entrust>
- [https://libre-soc.org/nlnet\\_2022\\_ongoing/](https://libre-soc.org/nlnet_2022_ongoing/)
- <https://libre-soc.org/nlnet/#faq>
- <https://git.libre-soc.org/?p=soc.git;a=tree;f=src/soc/experiment/formal;hb=HEAD>